

Physics Assignment

Hiba Muhammed
EE23BTECH11026

February 10, 2024

Problem Statement

A radio can tune over the frequency range of a portion of the MW broadcast band: (800 kHz to 1200 kHz). If its LC circuit has an effective inductance (L) and a variable capacitor with capacitance (C), what must be the range of C ?